



**Course Code:** CSE 210

**Course Title:** Digital Logic & System Design Lab

**Name of the Experiment:** Design and implement 4 bits ALU (Arithmetic Logic Unit

## Function table:

S2	S1	S0	Cin	ALU Functions	
0	0	0	0	A	AU Operations
0	0	0	1	A + 1	
0	0	1	0	A + B	
0	0	1	1	A + B + 1	
0	1	0	0	A + B'	
0	1	0	1	A - B	
0	1	1	0	A - 1 (Output carry effect)	
0	1	1	1	A	
1	0	0	x	OR	LU Operations
1	0	1	x	XOR	
1	1	0	x	AND	
1	1	1	x	NOT	

## Inputs and outputs:

There are 2 inputs A, B, and select function input S0, S1, S2, and Cin.

**Outputs:** A=1110 = 14, B =1010 =10; B'=0101=5

S2	S1	S0	Cin	ALU Functions	
0	0	0	0	A = 1110	<b>AU Operation</b>
0	0	0	1	A+1 = 1111	
0	0	1	0	A+B = 11000	
0	0	1	1	A+B+1 = 11001	
0	1	0	0	A+B' = 10011	
0	1	0	1	A-B = 0100	
0	1	1	0	A-1 = 1101	
0	1	1	1	A = 1110	
1	0	0	x	OR=1110	<b>LU Operation</b>
1	0	1	x	XOR=0100	
1	1	0	x	AND=1010	
1	1	1	x	NOT=0001	