

Course Title: Digital Logic and System Design

Course Code: CSE 210

Credit Hour: 1.5

Experiment No. 6

Experiment Name: Design a 4-bit ALU with 4-bit parallel adder (IC# 7483).

Tasks:

ALU - Arithmetic and Logical Unit

$$Xi = Ai + S2, S1', S0', Bi + S2, S1, S0', Bi'$$

$$Yi = S0, Bi + S1, Bi'$$

$$Zi = S2', Ci$$

Fall 21

Arithmetic -

Input - A, B

S2	S1	S0	Cin	Xi	Yi	Fi = (Xi xor Yi xor cin)	
0	0	0	0	Ai	0	A + 0 = A	Transfer
			1	Ai	0	A + 0 + 1 = A + 1	Increment
0	0	1	0	Ai	Bi	A+B (Add)	addition
			1	Ai	Bi	A+B+1 (Add)	Add with carry
0	1	0	0	Ai	Bi'	A + B' = A - B - 1	Add A with B'
			1	Ai	Bi'	A + B' + 1 = A - B	Subtraction
0	1	1	0	Ai	1	A + 2^n - 1	Decrement
			1	Ai	1	A + (2^n - 1) + 1 = A + 2^n	Transfer

⑦
⑧

Fall 21

Final Project for Lab presentation:

Marks : 30

1. Presentation → 15 (Simulation using any Simulator)
2. Design → 10
3. ~~Lab~~

Cout

Presentation date:

10.04.2022 > B₁, A₂

12.04.2022 > B₂, A₁

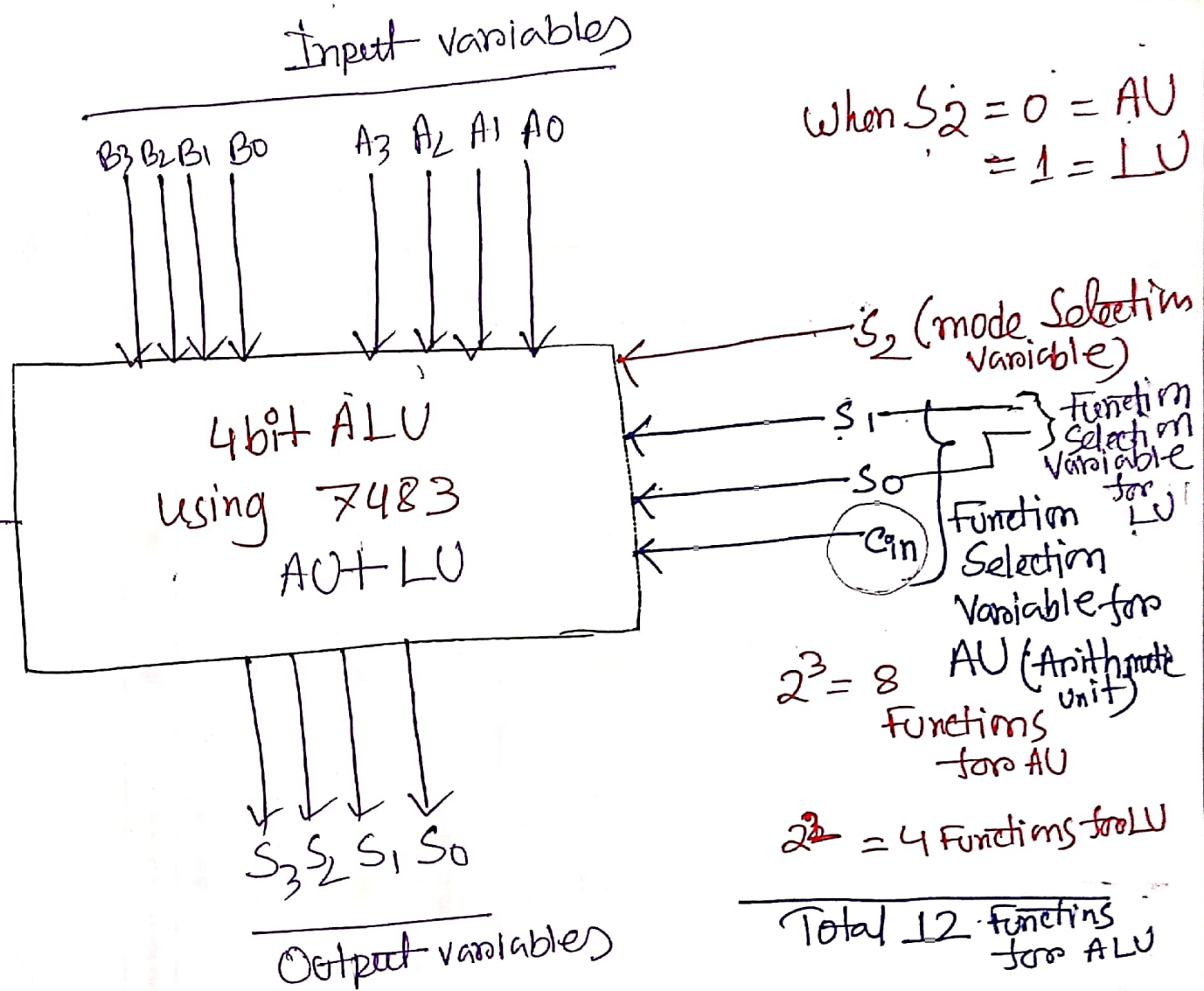


Fig: Block diagram for 4bit ALU.

S2	S1	S0	X_i	Y_i	$F = (X_i \text{ xor } Y_i)$	
1	0	0	$A_i + B_i$	0	$A + B \text{ (or)}$	OR
1	0	1	A_i	B_i	$A \text{ xor } B$	XOR
1	1	0	$A_i + B_i'$	B_i'	$A \cdot B$	AND
1	1	1	A_i	1	A'	NOT

Logic Expression

- 1) Problem Statement
- 2) Instruments (used in this experiment)
- 3) Truth table
- 4) Logic expression
- 5) Logic Diagram
- 6) Discussion

0111 = 11 - 11	1110
0001 = 2 - 1000	0110
	0110
	0001
	0000

Date :

03.04.22 → Register Transfer
10.04.22 → ALU Presentation
17.04.22 → Final Quiz

B₁ A₂

5.04.22 → Register Transfer
12.04.22 → ALU Presentation
19.04.22 → Final Quiz

B₂ A₁

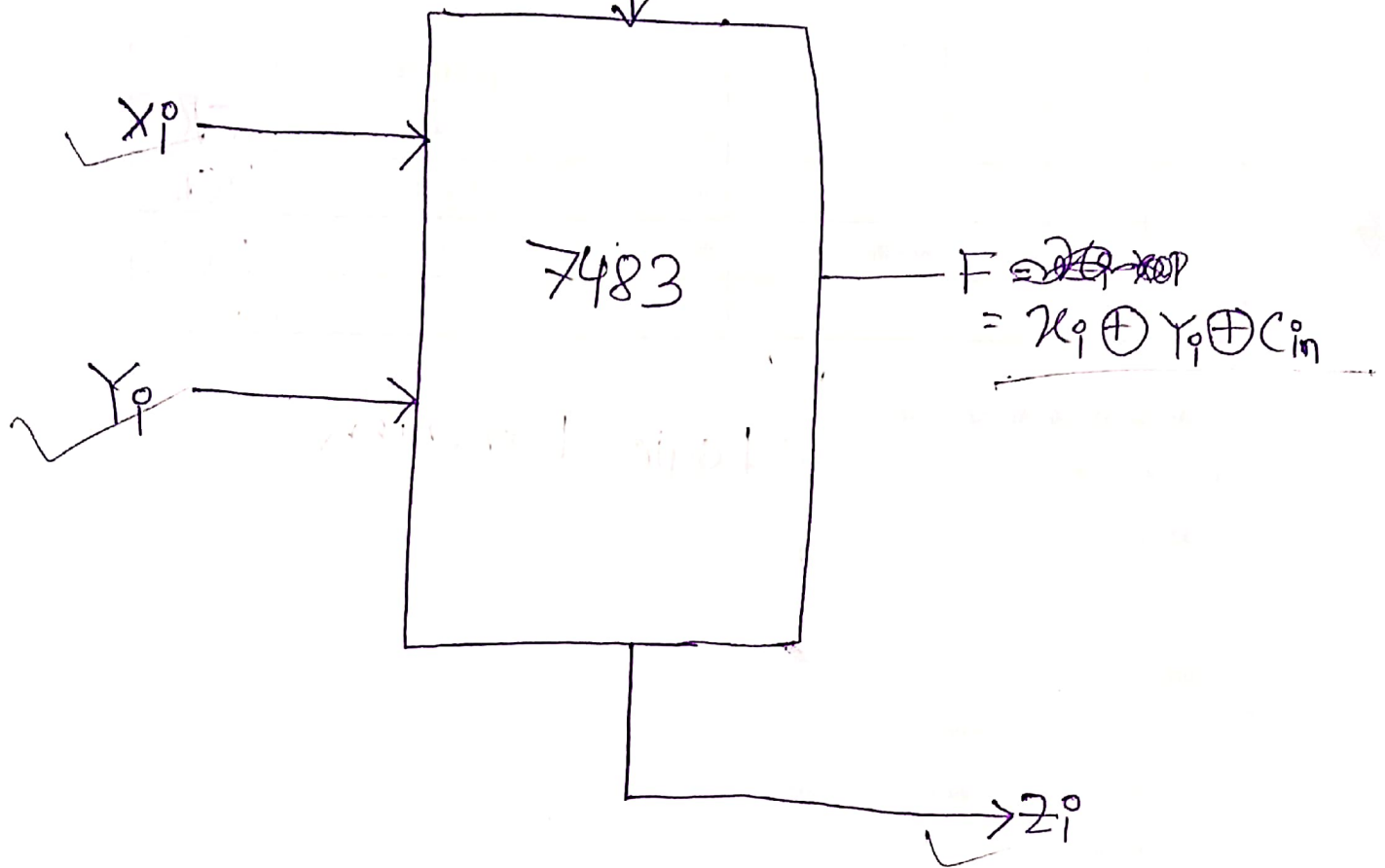


Fig: Block diagram of 7483

Example :

		A = 14 = 1110
		B = 8 = 1000
9	OR	1110
10	XOR	0110
11	AND	1000
12	NOT	0001

Give Examples for 12 functions :

① $F = A = 1110$

② $F = A + 1 = 1111$

③ $F =$

⑦ $F = A - 1 = 1101$

⑧ $F = A = 1110$